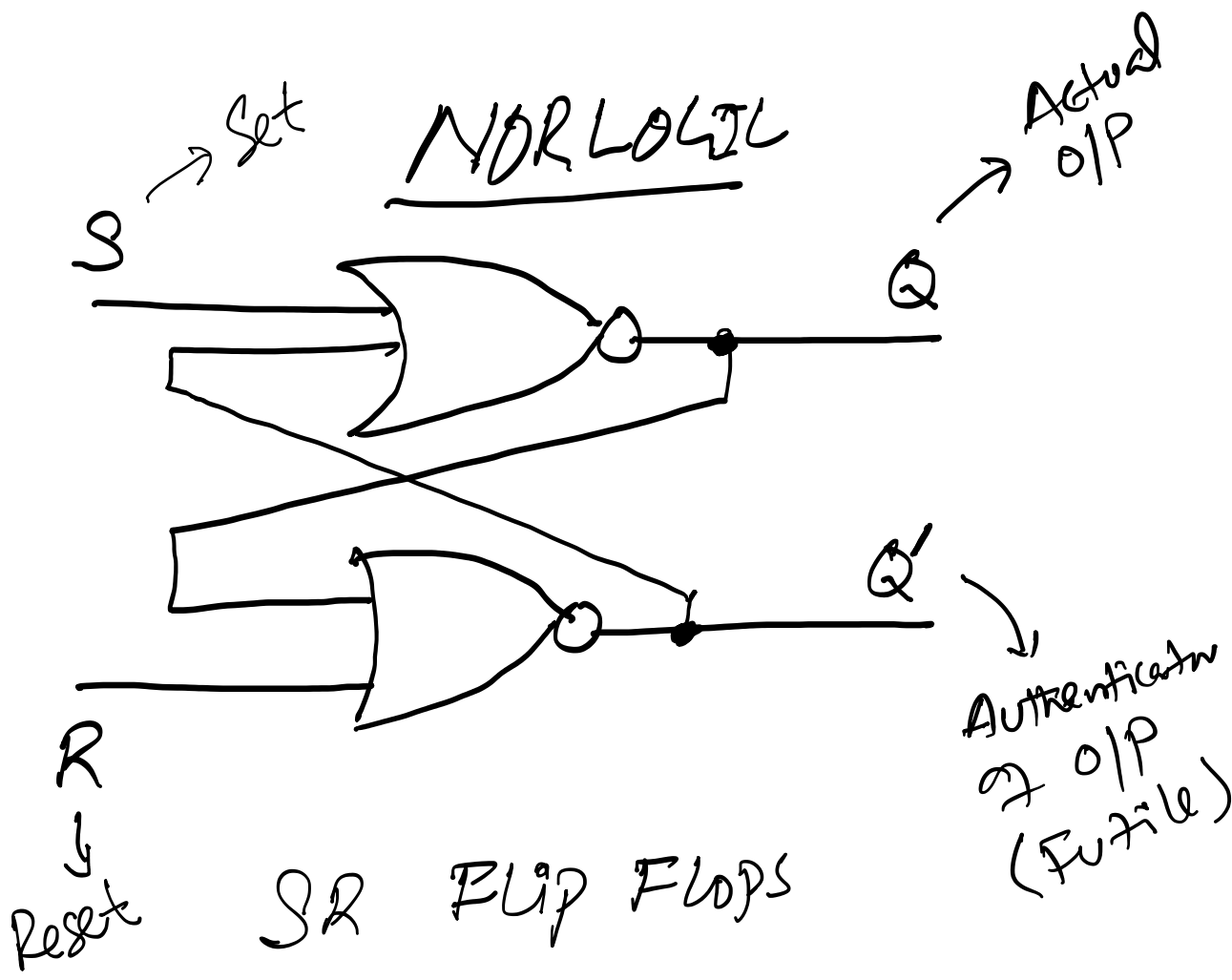



Flip Flops



S	R	Q	Q'	
1	0	1	0	Set
0	0	1	0	Latch
0	1	0	1	Reset
0	0	0	1	Latch
1	1	0	0	Race (Error)

- Flip flops are used to hold bits (data) in memory.


LIMITATIONS:	
1.	Single input change
2.	Error occurs.

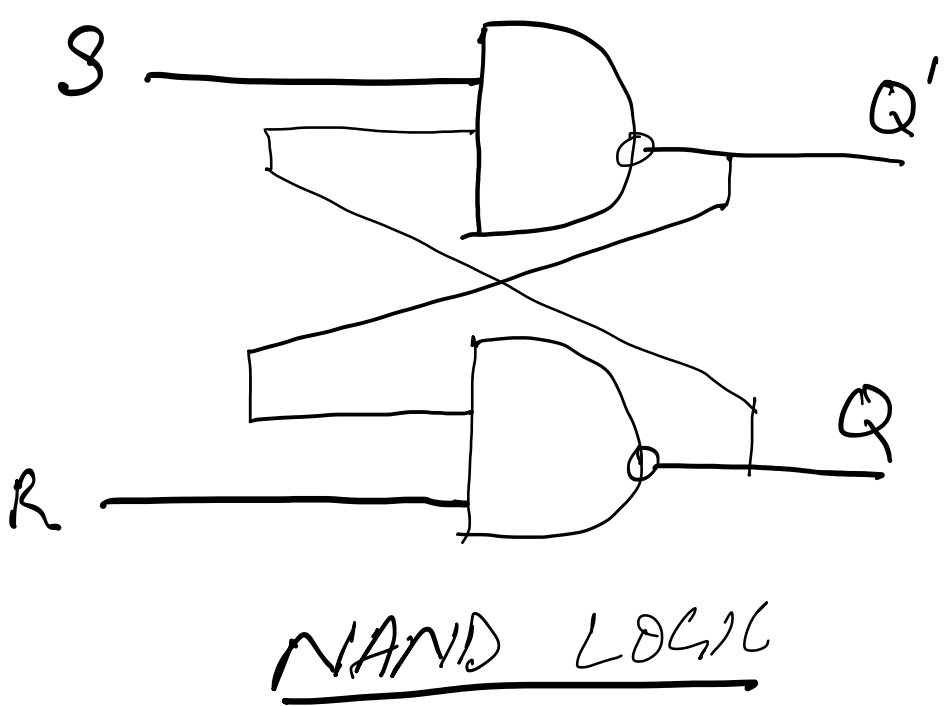

S	R	Q	Q'	
0	1	1	0	Set
1	1	1	0	Latch
1	0	0	1	Reset
1	1	0	1	Latch
0	0	1	1	Race (Error)

- These sequential circuits; which use their output as their new input.
- Only one change can be made to circuit input at a time; otherwise an error occurs.

JK Flip Flops:

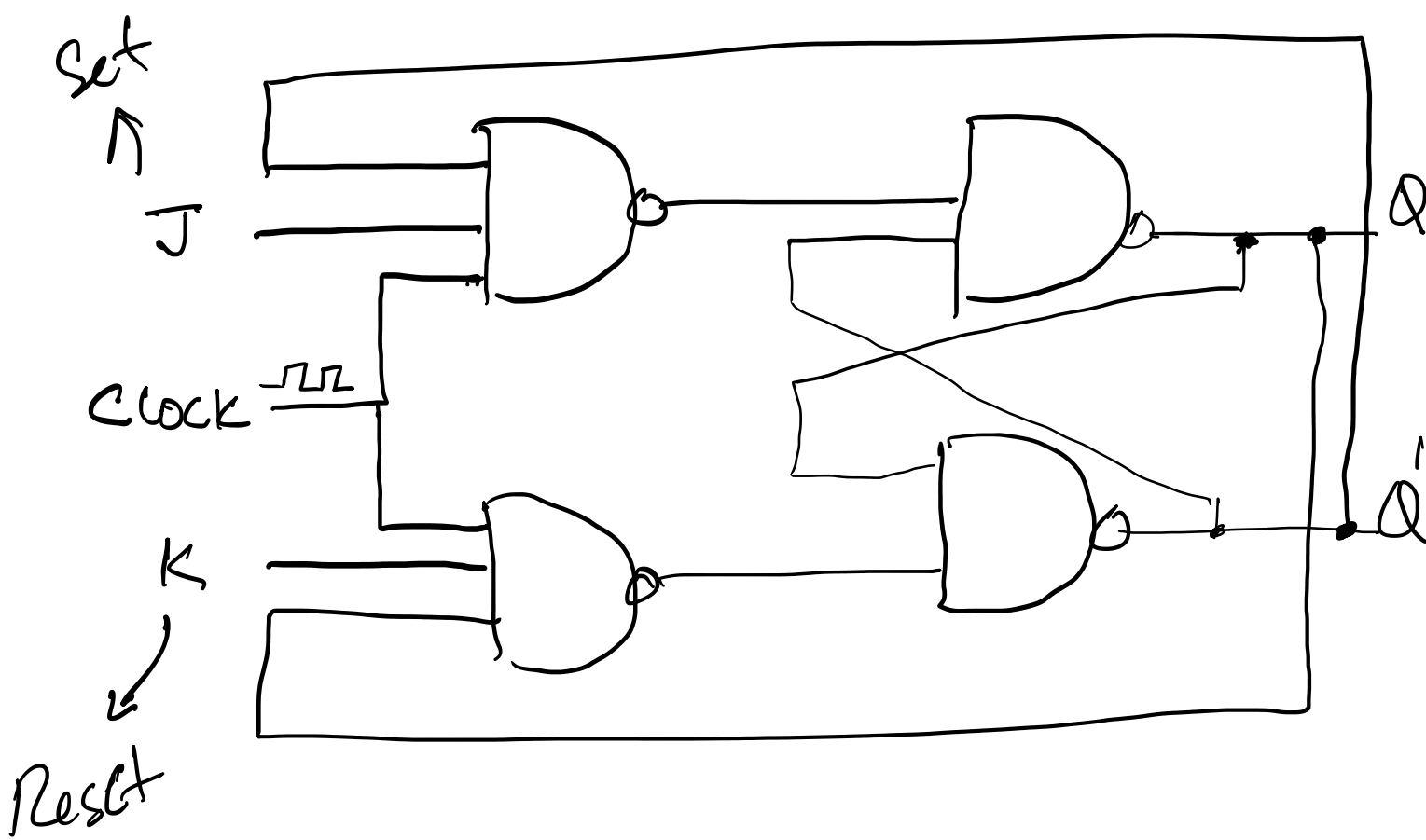

- It overcomes all weaknesses of SR Flip Flop
- No Race
- No Limitation of single input
- only works when clock produces high (↑) cycle.
- When two inputs are changed, a new operation of toggle/increase a bit occurs.

J	K	Clock	Q	Q'	
1	0	↑	1	0	Set
0	1	↑	0	1	Reset
0	0	↑	0	1	Latch
1	1	↑	1	0	Toggle