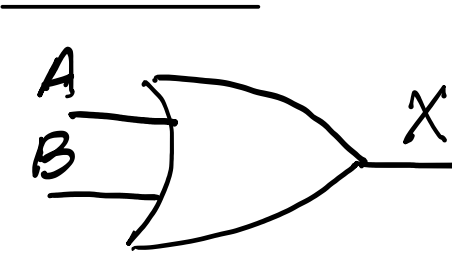
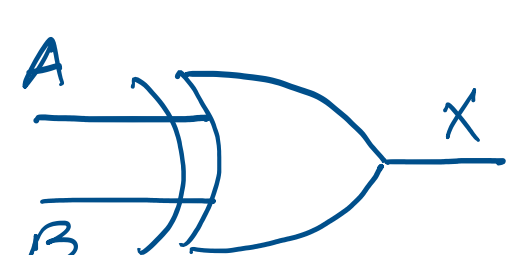
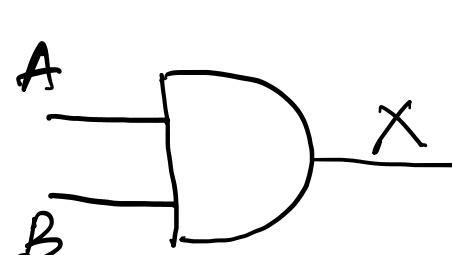
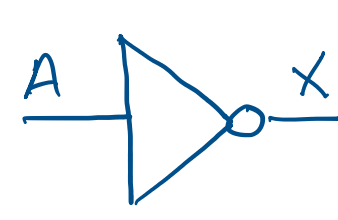
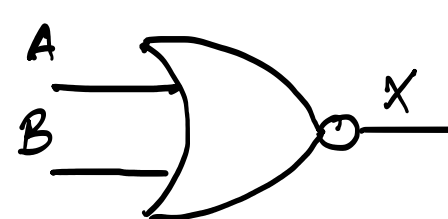



Why computer works in binary?

Computers are made of Logic Circuits, which take input in binary, so computer uses/knows only binary.

MIL. Symbols.	LOGIC	Operator	Statement	Logic Expression	Truth Table															
1. 	OR	+	$X = (A+B)$	$X=1$, IF (A OR B)	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	1																		
2. 	XOR	\oplus	$X = (A \oplus B)$	$X=1$, IF (A XOR B)	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		
3. 	AND	*	$X = (AB)$	$X=1$, IF (A AND B)	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																		
0	0	0																		
0	1	0																		
1	0	0																		
1	1	1																		
4. 	NOT Inverts	'	$X = A'$	$X=1$, IF NOT A	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																			
0	1																			
1	0																			

5.  NOR $(+)'$ $X = (A+B)'$ $X=1$, IF NOT (A OR B)

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

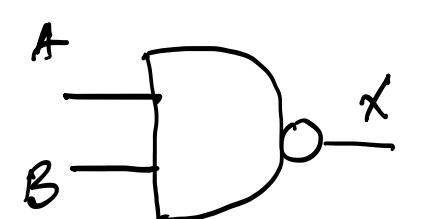6.  NAND $(*)'$ $X = (AB)'$ $X=1$, IF NOT (A AND B)

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

1. Used to create memories.

2. UNIVERSAL GATES.

- * Universal gates are used to create any other gate or circuit.
- * Building Blocks (Topic)

Steps to learn Logic Gates:

- ✓ 1. knowing logic gates.
- ✓ 2. Drawing proper circuits.
3. Mathematical statements.
4. Logic expressions.
5. Truth Tables and Real World Scenarios.
6. Building Blocks.

Circuit Drawing:

Proper circuits drawing:

1. No diagonal lines
2. No lines overlapping.
3. Proper gates' shapes.

